

Friday, March 24, 2023




HACKATRONIC

Hacks of Electronics

Windows Driver

64/32 Bit Driver Download

Driver Support One

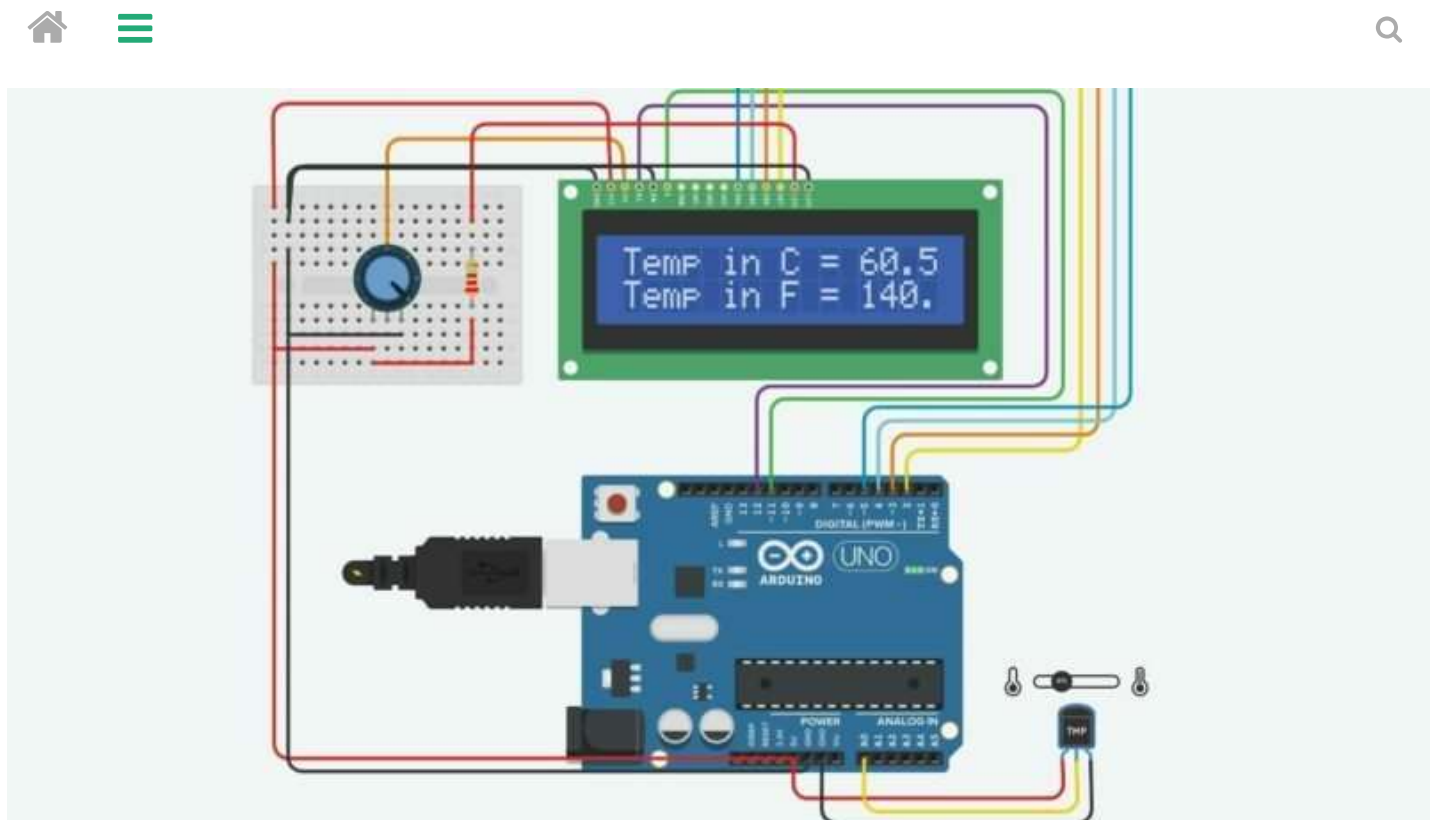[Arduino](#) [Arduino based projects](#) [Electronics tutorial](#)

Arduino with temperature sensor – Interfacing LCD and LM35

Start Download

Microsoft™ 64/32 Bit Driver Download


Driver Support

Download

Let's see how to interface Arduino with temperature sensor. LM35 is a three-terminal temperature sensing device. It is used to measure temperature in the range of -55°C to 150°C . It is a three-terminal device that produces an analog voltage proportional to the temperature of its surroundings. We can convert the analog output into digital using ADC. The sensitivity of LM35 is $10\text{mV/degree Celsius}$ it does not require any extra calibration (e.g. 300mV means 30°C). Its output is very precise. Supply voltage ranges from 4V to 30V .

Circuit Diagram of Arduino with temperature sensor:

Hackatronic.com

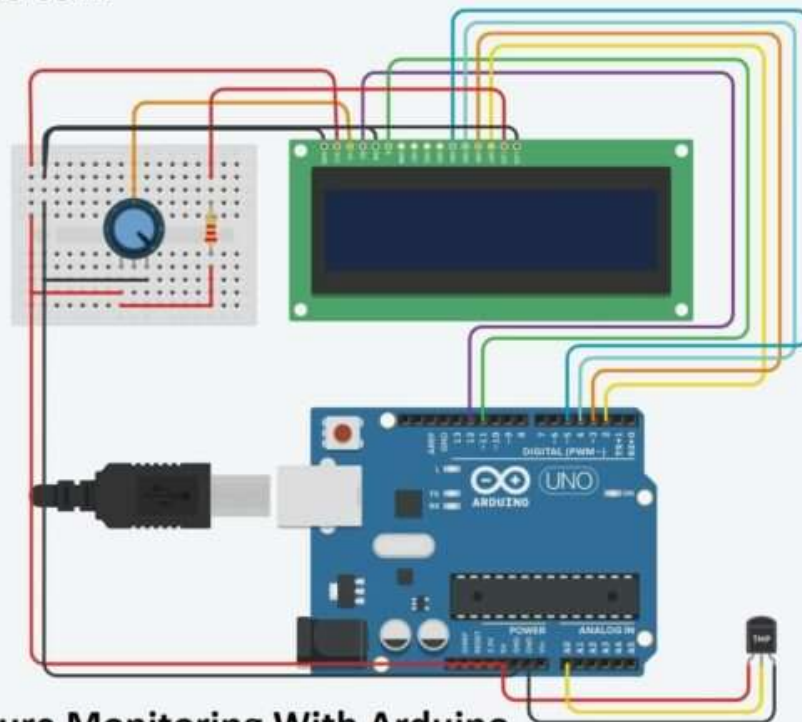



Components Required:

- Arduino UNO R3 board
- Variable resistor 10k Ω
- Resistor 220 Ω
- 8 bit LCD
- Mini breadboard
- LM35 temperature sensor
- Few wires & cable for power supply

Circuit connections:

The LM35 temperature sensor is powered by an Arduino board via VCC & GND pins.

The analog output pin of the LM35 temperature sensor is connected to the analog input pin A0 of Arduino.

10 K Ohm potentiometer controls the brightness of the panel.

The second pin is connected to pin 3 of the LCD.

First pin of potentiometer connected to + VCC.

Third pin of potentiometer connected to GND.

RS pin of LCD connects to digital pin 12 of Arduino UNO.

Pin E (Enable) connected to digital pin 11.

Pin D4 connects to pin number 5.

D5 pin connects to digital pin 4 of Arduino.

Pin D6 connects to digital pin 3.

Pin D7 connects to digital pin 2 of Arduino UNO.

R / W pin connected to the GND.

Pin 1 and pin 4 are connected to GND.

Pin 2 connected to + VCC.

The first and third pins of the potentiometer can be interchanged.

Working of Temperature sensor with code :

```
#include <LiquidCrystal.h>
```

```
float temp;
```

```
int sensor = A0;
```

```
float tempc;
```

```
float tempf;
```

```
LiquidCrystal lcd (12, 11, 5, 4, 3, 2);
```

The instance of the LiquidCrystal lcd shows LCD pins connected to the Arduino digital outputs.

```
void setup () {
```

```
// set the number of columns and the number of lines of lcd
```

```
lcd.begin (16, 2);
```

```
}
```

```
void loop () {  
temp=analogRead(sensor);
```

Read analog voltage from sensor and store it in a temporary float variable.

```
tempc=(temp*4.88)/10;
```

This line converts float value into °C.

```
tempf=(tempc*1.8)+32;
```

This line converts °C into Fahrenheit.

```
lcd.setCursor(0,0);  
lcd.print("Temp in C = ");  
lcd.println(tempc);
```


These two lines print Temperature value in °C.

```
lcd.setCursor(0,1);  
lcd.print("Temp in F = ");  
lcd.println(tempf);
```

Above two lines print value in Fahrenheit

```
}
```

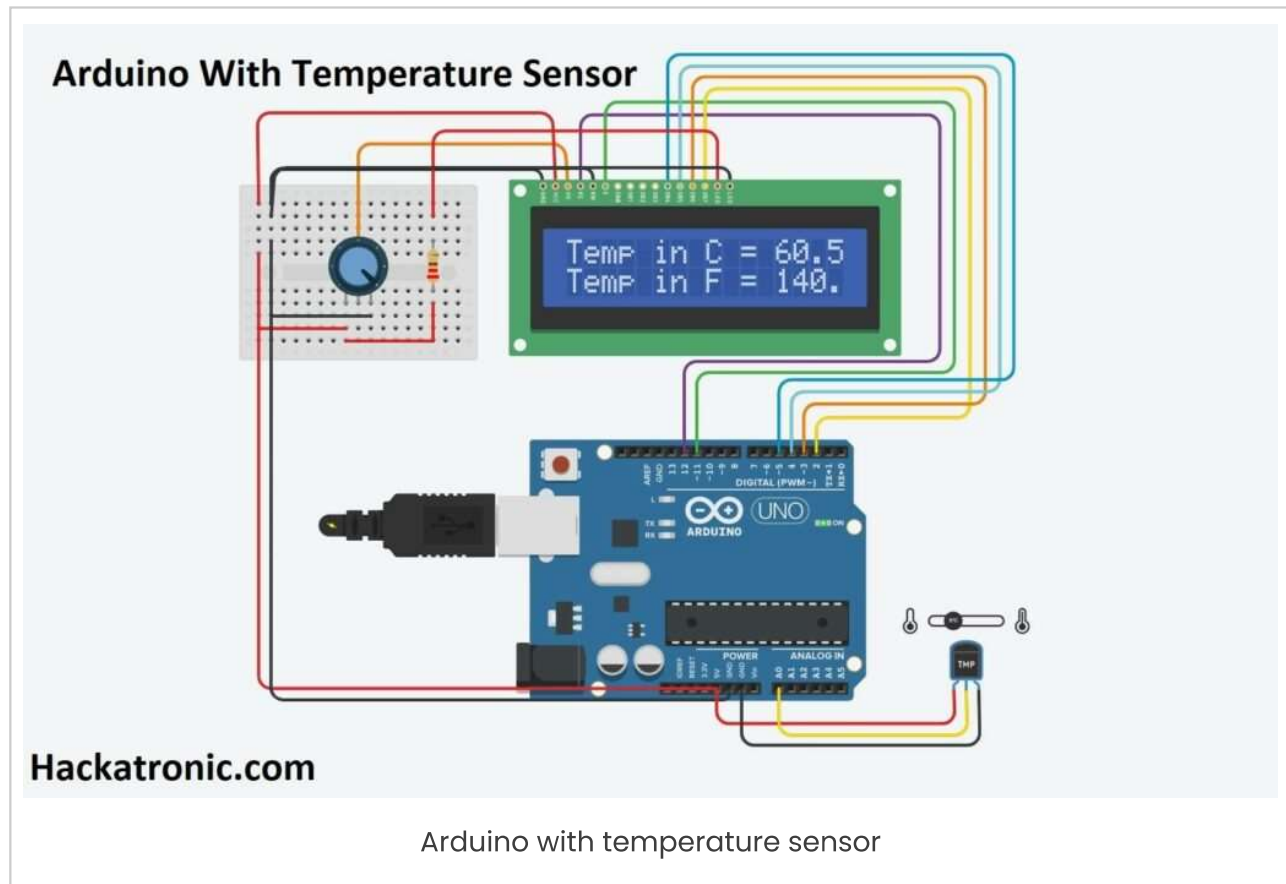Arduino with temperature sensor Final Output:



```
#include <LiquidCrystal.h>
int sensor = A0;
float temp;
float tempc;
float tempf;

LiquidCrystal lcd (12, 11, 5, 4, 3, 2);
void setup () {
  lcd.begin (16, 2);
}

void loop () {
  temp=analogRead(sensor);
  tempc=(temp*4.88)/10;
  tempf=(tempc*1.8)+32;
  lcd.setCursor(0,0);
  lcd.print("Temp in C = ");
  lcd.println(tempc);
```

```
lcd.setCursor(0,1);  
lcd.print("Temp in F = ");  
lcd.println(tempf);  
}
```

Here is the TinkerCAD Simulation of This project:

Conclusion:

- The above circuit is used to monitor the temperature in many places,
- In weather monitoring system.
- In farming fields
- Industrial places
- At home and anywhere there is a need for temperature data.

◆ Tagged arduino code for temperature sensor lm35 with lcd display, arduino lm35 temperature sensor with 7 segment display, arduino lm35 temperature sensor with i2c lcd display, arduino lm35 temperature sensor with led, arduino temperature sensor with leds and buzzer, arduino uno temperature and humidity sensor with lcd, arduino uno temperature sensor with lcd, Arduino with temperature sensor, how to connect temperature sensor with arduino, lm35 temperature sensor interfacing with arduino, temperature sensor with arduino uno, temperature sensor with lcd display arduino



Abhishek Singh

<https://hackatronic.com>

◀ Arduino LCD Progr...

What is Scaling of ... ▶

Leave a Reply

Your email address will not be published. Required fields are marked *

Comment *

Name *

Email *

Website

☐

Save my name,
email, and
website in this
browser for the
next time I
comment.

☐ Notify me of follow-up comments by email.

☐ Notify me of new posts by email.

Post Comment

This site uses Akismet to reduce spam. [Learn how your comment data is processed.](#)

TOPICS

📁 Arduino (3)

📁 Communication technologies (4)

📁 5G technology (1)

📁 Computer Science (4)

📁 Information Security (1)

📁 Accountability (1)

📁 Authenticity (1)

📁 Availability (1)

📁 CIA Triad (1)

📁 Confidentiality (1)

📁 Integrity (1)

📁 Non-Repudiation (1)

📁 Single Sign On (1)

📁 Federated Identity Management (1)

📁 Open Authorization (1)

📁 SAML (1)


📁 Identity Provider & Service Provider (1)

📁 IdP & SP (1)

📁 Security Assertion Markup Language (1)

📁 Sign In with Google (1)

📁 Open ID Connect (1)

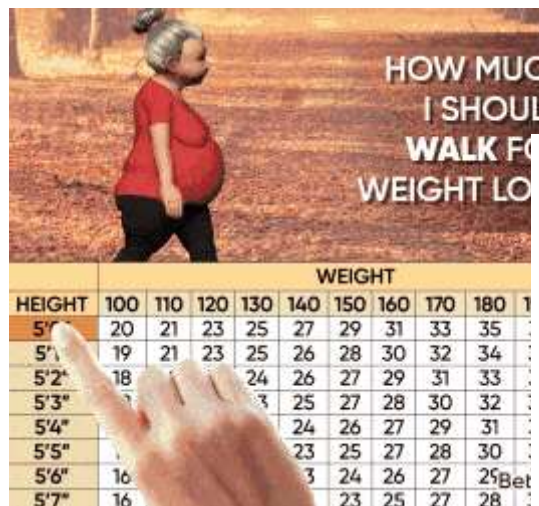

- 📁 Electronics tutorial (91)
- 📁 Arduino based projects (13)
- 📁 ESP32 (4)

- 📁 Counter Circuits (8)

- 📁 Counter ICs (2)

- 📁 Electronic devices (14)

- 📁 Electronics components (11)

- 📁 Active components (2)

- 📁 Passive components (2)

- 📁 Electronics project (14)

- 📁 Bc 547 transistor projects (4)

- 📁 Flip Flops (5)

- 📁 high frequency PCB design (1)

- 📁 Integrated circuits (ICs) (13)

- 📁 555 timer IC (5)

- 📁 Logic Gates (1)

- 📁 NOR Gate (1)

📁 NOR Gate Truth Table (1)

📁 NOT using NOR (1)

📁 Pin Diagram for 74LS02 (1)

📁 Universal NOR Gate (1)

📁 AND using NOR (1)

📁 OR using NOR (1)

📁 MOSFETs (1)

📁 Power supplies (7)

📁 5 volt DC power supply (1)

📁 Inverters (3)

📁 Protection Circuits (4)

📁 Raspberry Pi (3)

📁 Raspberry Pi IOT Projects (2)

📁 Types of Diode (6)

📁 Shockley Diode (1)

📁 Working of Diode (2)

📁 Zener Diode (1)



📁 Gadgets (2)

📁 Internet of things (4)

📁 IOT (4)

📁 OP-AMP tutorial (20)

📁 Opamp based project (5)

📁 Amplifier Projects (2)

📁 Operational amplifier basics (10)

📁 PCB Manufacturing (1)

📁 Tech one (3)

📁 Google (1)

📁 Google Drive (1)

📁 Google Drive Troubleshooting (1)

DATASHEET

Datasheet [Search](#)



RECENT COMMENTS

- Abhishek Singh on [Water Level Indicator and Pump Controller using Arduino](#)
- Atonu Halder on [Water Level Indicator and Pump Controller using Arduino](#)
- Abhishek Singh on [LM317 adjustable voltage regulator circuit](#)
- Ananya Kc on [LM317 adjustable voltage regulator circuit](#)
- Bert and on [Short Circuit Protection Using Relay For Batteries](#)

> [Arduino](#)

- > [ESP32](#)
- > [Raspberry Pi](#)
- > [Electronics components](#)
- > [OP-AMP tutorial](#)
- > [Counter Circuits](#)
- > [Flip Flops](#)
- > [Power supplies](#)
- > [Types of Diode](#)

SUBSCRIBE TO HACKATRONIC

Enter your email address and get all the new content in your mail.

Join 56 other subscribers

- > [Electronics tutorial](#)
- > [Electronics project](#)
- > [Integrated circuits \(ICs\)](#)
- > [Resistor color code calculator](#)
- > [About Hackatronic](#)
- > [Contact Us](#)
- > [Privacy policy](#)

> Disclaimer

2022 hackatronic.com | Newspaper Lite by themecentury.